


Tutorial Assignments: Analog Signal Processing (EE60032),

Department of Electrical Engineering, Indian Institute of Technology, Kharagpur

Faculty: Ashis Maity

Session: Autumn 2018

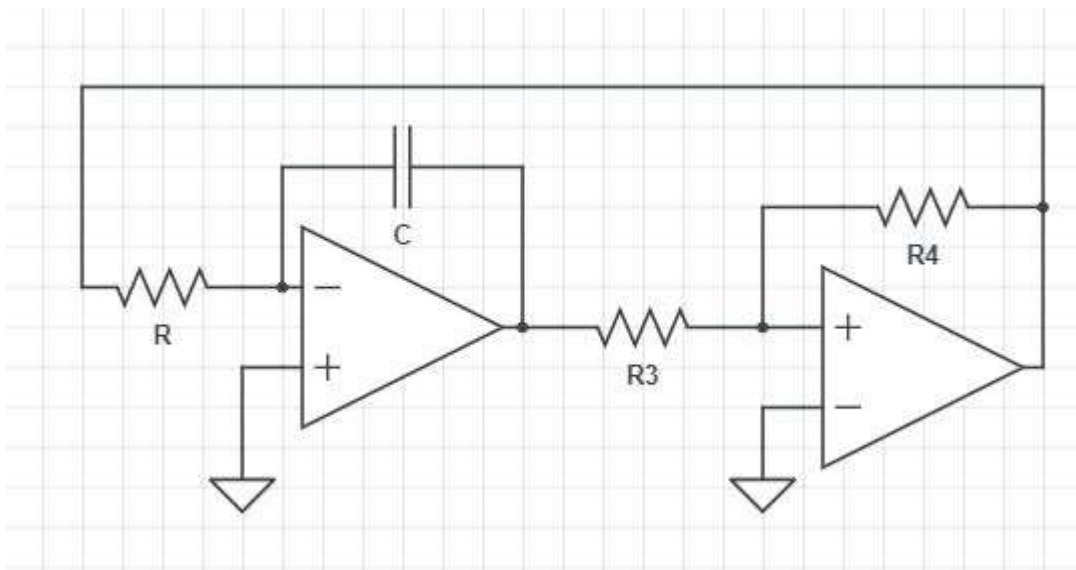1. Consider the circuit in the below figure which generates triangular and square waveforms. If the op-amp has a saturation voltage of  $\pm 10\text{V}$  and if a capacitor  $C=0.01\mu\text{F}$  is used. Find out the value of  $R$ ,  $R_3$  and  $R_4$  such that the frequency of oscillation is  $1\text{ kHz}$  and the triangular waveform has  $10\text{V}$  peak to peak amplitude. [Ans:  $R=50\text{k}\Omega$ ,  $R_3=10\text{k}\Omega$ ,  $R_4=20\text{k}\Omega$ ]



2. In type-1 PLL, determine the change in dc control voltage  $V_{\text{control}}$  during lock, if the input signal frequency  $f_{\text{in}}=20\text{kHz}$ , the free running frequency is  $21\text{kHz}$  and the gain of the VCO  $K_{\text{VCO}}= 4\text{ kHz/V}$ . [Ans:  $0.25\text{V}$ ]